

姓名   卢   班级   \*\*\*\*\*   学号   \*\*\*\*\*  

实验日期            节次            教师签字            成绩           

## 基于 BASYS2 的简易数字秒表

### 1. 实验目的

- ①熟悉 Verilog 语言的语法和使用。
- ②理解并运用模块化设计思想进行设计。
- ③掌握 Moore 型状态机的设计方法。
- ④能够利用 ISE 软件开发简单的 FPGA 应用。

### 2. 总体设计方案或技术路线

#### 1) 确定设计要求

设计一个数字秒表，计时范围为 0~9min59.9s，通过四位数码管显示示值，具有复位和启停按钮，实现复位和计时/停止功能，且计时溢满时自动停止。

#### 2) 制定设计方案

总体采用模块化设计方法，将任务按功能特性分解，让每个模块负责一个相对独立的功能：

0.主模块：对接口进行包装，并将各个子模块连接起来。

1.时钟分频模块：对内部时钟进行分频，提供一个较低频的时钟用于驱动各时序模块。

2.控制模块：核心部分，响应操作并控制计时。

控制模块的基本行为可以使用一个 Moore 型状态机描述。状态机有四个状态：RESET（复位）、STOP（停止）、RUN（计时进行）和 OVERFLOW（溢出），并通过三个输入控制：rst（复位）、toggle（启停）和 overflow（溢出标志）。控制模块的状态转换示意图如图 1。

3.数码管显示模块：将输入转换为数码管显示。

4.按键检测模块：检测按键输入响应，主要是消抖，以及保证启停按键只在按下时响应（边沿触发）。

#### 3) 编写程序并下载验证。

 


图 1：控制模块的状态转换示意图

### 3. 实验电路图

因采用 Verilog 语言进行编写的程序，故没有实验电路图。

### 4. 仪器设备名称、型号

Xilinx BASYS2 开发板

### 5. 理论分析或仿真分析结果

主要对作为核心的控制模块进行仿真验证。

为了便于显示仿真结果，仿真所用的时钟输入周期为  $5\mu\text{s}$ ，而模块设计所期待的时钟输入周期为  $5\text{ms}$ （实际由时钟分频模块产生），故仿真显示的时间尺度比实际小了  $10^3$ 。

图 2 是对复位、启停功能的验证。

 


图 2：复位、启停功能仿真波形

图 3 是对计时功能和特性的验证。

 


图 3：计时功能仿真波形

## 6. 详细实验步骤及实验结果数据记录（包括各仪器、仪表量程及内阻的记录）

- (1) 根据设计方案，使用 Verilog 语言编写程序（程序源码见附录）。
- (2) 将编写好的程序下载进开发板中，按设计要求对功能进行验证。

## 7. 实验结论

成功利用 BASYS2 开发板按实现了一个符合预期设计要求的简易秒表。

## 8. 实验中出现的問題及解决对策

- ①问题：开始设计时分频驱动时钟频率太低，导致数码管扫描周期过长，目视有明显闪烁。  
解决对策：调整参数，提高分频模块输出的时钟频率。

②问题：编写程序时，想当然地将一个模块的输出连接到 `reg` 类型的信号上，导致综合失败。

解决对策：引入 `wire` 类型的中间信号，在 `always` 语句中对 `reg` 类型的信号进行赋值。

## 9. 本次实验的收获和体会、对电路实验室的意见或建议

锻炼了使用 `FPGA` 进行开发的能力，加深了对模块化设计、有限状态机等思想的理解。

## 10. 参考文献

[1] 杨春玲, 王淑娟主编. 数字电子技术基础[M]. 2 版. 北京: 高等教育出版社, 2017

## 附录：程序源码

主模块 - main.v

```
module main(
    input clk,           // 50MHz
    input [1:0] btn,     // 按钮
    output [3:0] an,     // 数码管位选
    output ca,          // 数码管段选
    output cb,
    output cc,
    output cd,
    output ce,
    output cf,
    output cg,
    output dp
);

    wire clk5ms;
    wire rst, toggle;
    wire [3:0] dsec;
    wire [3:0] sec0;
    wire [3:0] sec1;
    wire [3:0] min;

    clkGen u1(
        .clk50MHz_i (clk),
        .clk5ms_o   (clk5ms)
    );

    controller u2(
        .rst_i      (rst),
        .toggle_i   (toggle),
        .clk_i       (clk5ms),
        .dsec_o      (dsec),
        .sec0_o      (sec0),
        .sec1_o      (sec1),
        .min_o       (min)
    );

    digitDisplay u3(
        .bcd_i0      (dsec),
        .bcd_i1      (sec0),
        .bcd_i2      (sec1),
        .bcd_i3      (min),
```

```

.dp_i      (4'b0101),
.clk_i     (clk5ms),
.sel_o     (an),
.a_o       (ca),
.b_o       (cb),
.c_o       (cc),
.d_o       (cd),
.e_o       (ce),
.f_o       (cf),
.g_o       (cg),
.dp_o      (dp)
);

keyPress u4(
.key_i     (btn[1]),
.pressed_o (rst),
.clk_i     (clk5ms)
);

keyClick u5(
.key_i     (btn[0]),
.clicked_o (toggle),
.clk_i     (clk5ms)
);

endmodule

```

时钟分频模块 - clkGen.v

```

module clkGen(
    input clk50MHz_i,
    output clk5ms_o
);

    parameter TIMES = 250_000; // 5ms

    reg [18:0] cnt; // see also TIMES
    reg out;

    initial
    begin
        cnt <= 0;
        out <= 0;
    end

```

```

always@(posedge clk50MHz_i)
begin
    if(cnt < (TIMES-1))
        cnt <= cnt +1;
    else
        cnt <= 0;
end

always@(posedge clk50MHz_i)
begin
    if(cnt == 0)
        out <= 1;
    else if(cnt == (TIMES/2))
        out <= 0;
    else
        out <= out;
end

assign clk5ms_o = out;

endmodule

```

控制模块 – controller.v

```

module controller(
    input rst_i,
    input toggle_i,
    input clk_i,          // 5ms
    output [3:0] dsec_o,
    output [3:0] sec0_o,
    output [3:0] sec1_o,
    output [3:0] min_o
);

parameter RESET = 0, STOP = 1, RUN = 2, OVERFLOW = 3;
parameter BASE = 20; // 100ms

reg [3:0] dsec_reg;
reg [3:0] sec0_reg;
reg [3:0] sec1_reg;
reg [3:0] min_reg;
reg [1:0] current_state, next_state;

wire overflow;

```

```

initial
begin
    current_state <= RESET;
end

always@(posedge clk_i)
begin
    current_state <= next_state;
end

always@(current_state or rst_i or toggle_i or overflow)
begin
    case(current_state)
    RESET:
    begin
        if(rst_i)
            next_state <= RESET;
        else if(toggle_i)
            next_state <= RUN;
        else
            next_state <= STOP;
    end
    STOP:
    begin
        if(rst_i)
            next_state <= RESET;
        else if(toggle_i)
            next_state <= RUN;
        else if(overflow)
            next_state <= OVERFLOW;
        else
            next_state <= STOP;
    end
    RUN:
    begin
        if(rst_i)
            next_state <= RESET;
        else if(toggle_i)
            next_state <= STOP;
        else if(overflow)
            next_state <= OVERFLOW;
        else
            next_state <= RUN;
    end
end

```



```

OVERFLOW:
begin
    if(rst_i || toggle_i)
        next_state <= RESET;
    else
        next_state <= OVERFLOW;
    end
default:
    next_state <= RESET;
endcase
end

reg [4:0] basecnt; // see also BASE
always@(posedge clk_i)
begin
    case(current_state)
    RESET:
        basecnt <= 0;
    STOP:
        basecnt <= basecnt;
    RUN:
    begin
        if(basecnt == (BASE-1))
            basecnt <= 0;
        else
            basecnt <= basecnt + 1;
        end
    OVERFLOW:
        basecnt <= 0;
    endcase
end

wire carry_dsec; // 0.1s
assign carry_dsec = ((dsec_reg == 9) && (basecnt == (BASE-1)));
always@(posedge clk_i)
begin
    case(current_state)
    RESET:
        dsec_reg <= 0;
    STOP:
        dsec_reg <= dsec_reg;
    RUN:
    begin
        if(carry_dsec)

```

```

        dsec_reg <= 0;
    else if(basecnt == (BASE-1))
        dsec_reg <= dsec_reg + 1;
    else
        dsec_reg <= dsec_reg;
end
OVERFLOW:
    dsec_reg <= 9;
endcase
end

wire carry_sec0; // 1s
assign carry_sec0 = (carry_dsec && (sec0_reg == 9));
always@(posedge clk_i)
begin
    case(current_state)
    RESET:
        sec0_reg <= 0;
    STOP:
        sec0_reg <= sec0_reg;
    RUN:
    begin
        if(carry_sec0)
            sec0_reg <= 0;
        else if(carry_dsec)
            sec0_reg <= sec0_reg + 1;
        else
            sec0_reg <= sec0_reg;
    end
    OVERFLOW:
        sec0_reg <= 9;
    endcase
end

wire carry_sec1; // 10s
assign carry_sec1 = (carry_sec0 && (sec1_reg == 5));
always@(posedge clk_i)
begin
    case(current_state)
    RESET:
        sec1_reg <= 0;
    STOP:
        sec1_reg <= sec1_reg;
    RUN:

```

```

begin
    if(carry_sec1)
        sec1_reg <= 0;
    else if(carry_sec0)
        sec1_reg <= sec1_reg + 1;
    else
        sec1_reg <= sec1_reg;
    end
    OVERFLOW:
        sec1_reg <= 5;
    endcase
end

// min
assign overflow = (carry_sec1 && (min_reg == 9));
always@(posedge clk_i)
begin
    case(current_state)
    RESET:
        min_reg <= 0;
    STOP:
        min_reg <= min_reg;
    RUN:
    begin
        if(overflow)
            min_reg <= 9; // hold on
        else if(carry_sec1)
            min_reg <= min_reg + 1;
        else
            min_reg <= min_reg;
        end
    OVERFLOW:
        min_reg <= 9;
    endcase
end

assign dsec_o = dsec_reg;
assign sec0_o = sec0_reg;
assign sec1_o = sec1_reg;
assign min_o  = min_reg;

endmodule

```

# 数码管显示模块 – digitDisplay.v

```
module digitDisplay(  
    input [3:0] bcd_i0, // 输入 BCD8421 码  
    input [3:0] bcd_i1,  
    input [3:0] bcd_i2,  
    input [3:0] bcd_i3,  
    input [3:0] dp_i,    // 小数点控制  
    input clk_i,         // 5ms  
    output [3:0] sel_o, // 数码管位选输出, 低电平有效  
    output a_o,          // 数码管段选输出  
    output b_o,  
    output c_o,  
    output d_o,  
    output e_o,  
    output f_o,  
    output g_o,  
    output dp_o  
);  
  
    reg [3:0] sel_reg;  
    reg dp_reg;  
    reg [3:0] bcd_reg;  
    reg [1:0] tubeSel;  
  
    always@(posedge clk_i)  
    begin  
        case(tubeSel)  
            2'd0:  
                begin  
                    sel_reg <= 4'b0111;  
                    dp_reg <= dp_i[0];  
                    bcd_reg <= bcd_i0;  
                end  
            2'd1:  
                begin  
                    sel_reg <= 4'b1011;  
                    dp_reg <= dp_i[1];  
                    bcd_reg <= bcd_i1;  
                end  
            2'd2:  
                begin  
                    sel_reg <= 4'b1101;  
                    dp_reg <= dp_i[2];  
                    bcd_reg <= bcd_i2;  
                end  
        endcase  
    end  
end
```

```

        end
        2'd3:
        begin
            sel_reg <= 4'b1110;
            dp_reg <= dp_i[3];
            bcd_reg <= bcd_i3;
        end
    endcase

    tubeSel <= tubeSel +1;
end

assign sel_o = sel_reg;
digitSeg u1(
    .bcd_i      (bcd_reg),
    .a_o        (a_o),
    .b_o        (b_o),
    .c_o        (c_o),
    .d_o        (d_o),
    .e_o        (e_o),
    .f_o        (f_o),
    .g_o        (g_o)
);
assign dp_o = dp_reg;

endmodule

```

#### 数码管段码译码模块 – digitSeg.v

```

module digitSeg(
    input [3:0] bcd_i, // 输入 BCD8421 码
    output a_o,        // 数码管段选，低电平有效
    output b_o,
    output c_o,
    output d_o,
    output e_o,
    output f_o,
    output g_o
);

assign {a_o,b_o,c_o,d_o,e_o,f_o,g_o} =
    (bcd_i == 4'd0) ? 7'b0000001 :
    (bcd_i == 4'd1) ? 7'b1001111 :
    (bcd_i == 4'd2) ? 7'b0010010 :
    (bcd_i == 4'd3) ? 7'b0000110 :

```

```

(bcd_i == 4'd4) ? 7'b1001100 :
(bcd_i == 4'd5) ? 7'b0100100 :
(bcd_i == 4'd6) ? 7'b0100000 :
(bcd_i == 4'd7) ? 7'b0001111 :
(bcd_i == 4'd8) ? 7'b0000000 :
(bcd_i == 4'd9) ? 7'b0000100 :
7'bx;

```

```
endmodule
```

按键按下检测模块（电平触发） – keyPress.v

```

module keyPress(
    input key_i,          // 高电平有效
    output pressed_o,     // 高电平有效
    input clk_i           // 5ms
);

    parameter DURATION = 10; // 50ms

    reg [3:0] cnt; // see also: DURATION

    initial
    begin
        cnt <= 0;
    end

    always@(posedge clk_i)
    begin
        if(key_i == 1)
        begin
            if(cnt < DURATION)
                cnt <= cnt + 1;
            else
                cnt <= DURATION;
        end
        else
            cnt <= 0;
    end

    assign pressed_o = (cnt == DURATION);

endmodule

```

按键点击检测模块（边沿触发） – keyClick.v

```
module keyClick(  
    input key_i,  
    output clicked_o,  
    input clk_i  
);  
  
    wire pressed;  
    reg current, post;  
  
    always@(posedge clk_i)  
    begin  
        current <= pressed;  
    end  
  
    always@(posedge clk_i)  
    begin  
        post <= current;  
    end  
  
    keyPress u1(  
        .key_i      (key_i),  
        .pressed_o  (pressed),  
        .clk_i      (clk_i)  
    );  
  
    assign clicked_o = (post == 0) && (current == 1);  
  
endmodule
```

约束文件 port.ucf

```
NET "clk" TNM_NET = clk;  
TIMESPEC TS_CLK = PERIOD "clk" 20ns high 50%;  
  
NET "clk" LOC = B8;  
  
NET "btn<0>" LOC = G12;  
NET "btn<1>" LOC = C11;  
  
NET "ca" LOC = L14;  
NET "cb" LOC = H12;  
NET "cc" LOC = N14;  
NET "cd" LOC = N11;  
NET "ce" LOC = P12;
```

```
NET "cf" LOC = L13;
```

```
NET "cg" LOC = M12;
```

```
NET "dp" LOC = N13;
```

```
NET "an<0>" LOC = K14;
```

```
NET "an<1>" LOC = M13;
```

```
NET "an<2>" LOC = J12;
```

```
NET "an<3>" LOC = F12;
```